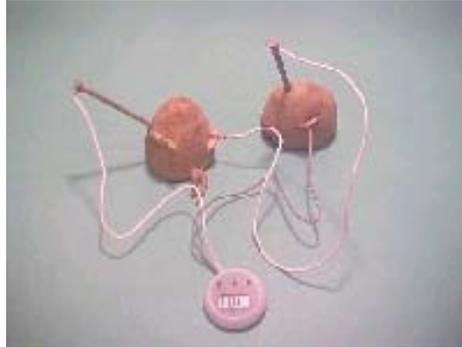


# BIOMASS: POTATO POWER



Curriculum: Biomass Power (organic chemistry, chemical/carbon cycles, plants, energy resources/transformations)

Grade Level: Grades 2 to 3


Small groups (3 to 4)

Time: 30 to 40 minutes

Summary: Students assemble a potato battery that will power a digital clock. This shows the connection between renewable energy from biomass and its application.

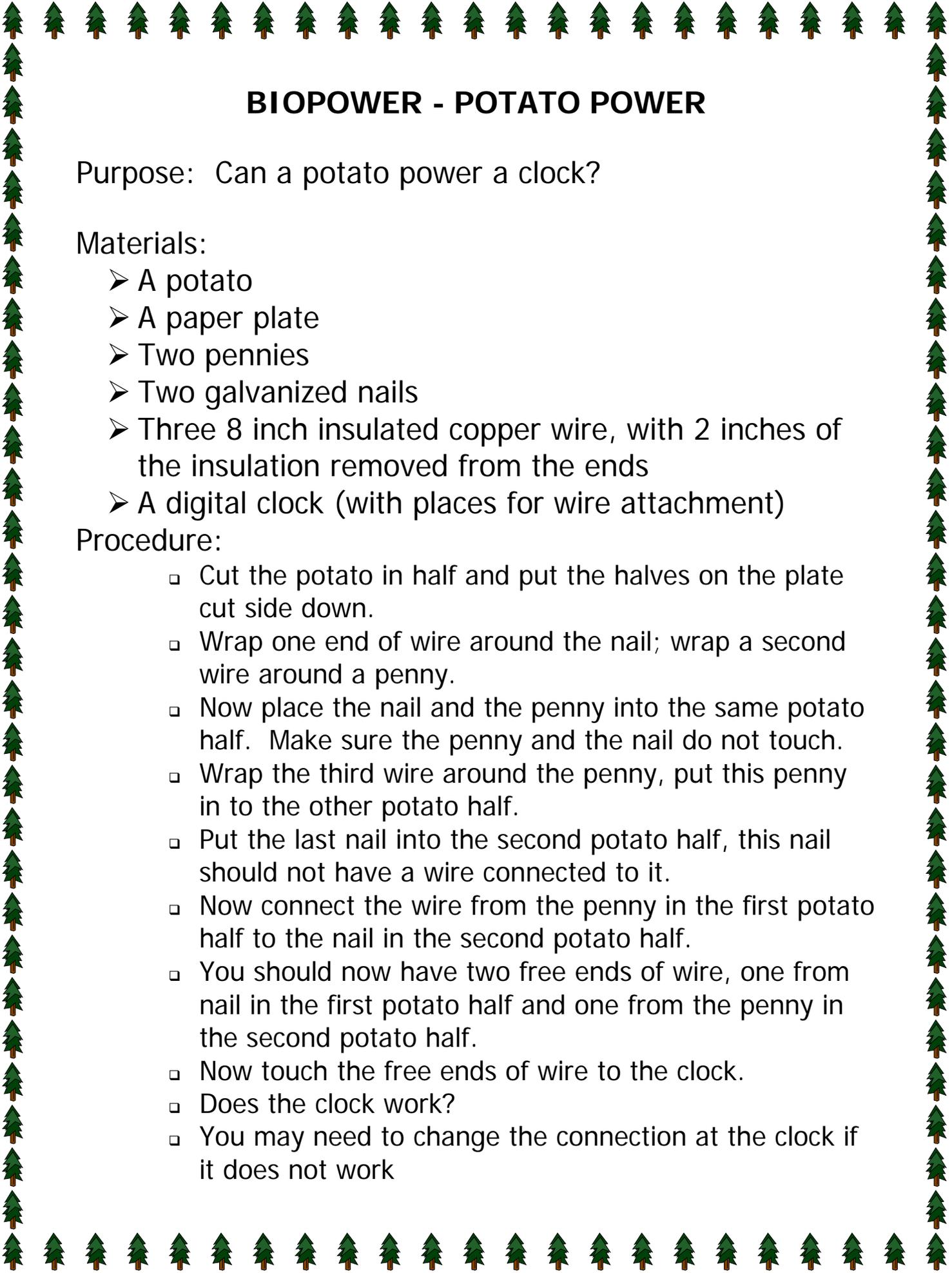Provided by the Department of Energy's  
National Renewable Energy Laboratory  
and BP America Inc.





## BIOPOWER - POTATO POWER

Purpose: Can a potato power a clock?

Materials:

- A potato
- A paper plate
- Two pennies
- Two galvanized nails
- Three 8 inch insulated copper wire, with 2 inches of the insulation removed from the ends
- A digital clock (with places for wire attachment)

Procedure:

- ❑ Cut the potato in half and put the halves on the plate cut side down.
- ❑ Wrap one end of wire around the nail; wrap a second wire around a penny.
- ❑ Now place the nail and the penny into the same potato half. Make sure the penny and the nail do not touch.
- ❑ Wrap the third wire around the penny, put this penny in to the other potato half.
- ❑ Put the last nail into the second potato half, this nail should not have a wire connected to it.
- ❑ Now connect the wire from the penny in the first potato half to the nail in the second potato half.
- ❑ You should now have two free ends of wire, one from nail in the first potato half and one from the penny in the second potato half.
- ❑ Now touch the free ends of wire to the clock.
- ❑ Does the clock work?
- ❑ You may need to change the connection at the clock if it does not work

